

# Design and Implementation of Buck-Boost Converter

A Voltage Mode Control Approach for  
DC-DC Converters

Satyam Singh  
IIT Ropar

# Introduction

- • Buck-Boost Converter provides stable voltage output for variable input sources.
- • Combines a Boost and Synchronous Buck converter.
- • Applications: Portable devices, renewable energy systems, EV charging.

# Design of Buck-Boost Converter

- • Circuit Design Overview
- • Key Components:
  - - Switches: S1, S2
  - - Inductors: L1, L2
  - - Capacitors: C1, C2, Co
- • Specifications:
  - - Input Voltage: 10V-16V
  - - Output Voltage: 12V
  - - Load Current: 2A

# Working Principle

- • Mode I (S1 ON, S2 OFF):
  - - C1 charges, L1 magnetizes.
  - - C2 discharges, L2 magnetizes.
- • Mode II (S1 OFF, S2 ON):
  - - L1 demagnetizes, C2 charges.
  - - Energy transfer to output.

# Voltage Conversion

- • Voltage conversion ratio:  $V_o/V_{in} = D/(1-D)$
- • Buck Mode: Output Voltage < Input Voltage  
( $D < 0.5$ )
- • Boost Mode: Output Voltage > Input Voltage  
( $D > 0.5$ )

# Simulation Results

- • MATLAB Simulation Output:
  - - Buck Mode: 16V input, 12V output.
  - - Boost Mode: 11V input, 12V output.
- • Stable output voltage achieved.

# Experimental Results

- • Buck Mode: 16V input, 12V output.
- • Boost Mode: 11V input, 12V output.
- • Dynamic response for step input changes.

# Conclusion

- • Buck-Boost converter provides a simple and efficient solution for variable input voltages.
- • Ensures system stability and fast transient response.
- • Suitable for low-power portable applications.